



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE113|Basic Electronics

Lab :4

Student Name: Dheeraj
Roll No.:2020194
Date:11-07-21

Aim: *. Observe the step response of the RLC circuit on LTspice and adjust the parameters so that an underdamped response of the series RLC circuit is obtained .Observe and trace the response.

* From the traced response, obtain the period of oscillation, time constant and peak overshoot and compare these values with theoretically calculated values.

* Adjust the parameter values so that a critical response of the series RLC circuit is obtained.

* Compare the critical resistance with theoretically calculated value.

.


Components: Resistor, Capacitor, Inductor,wires, Voltage source, ground.

Software/Tools Used :

- LT Spice

Theoretical Calculation :

Lab-4

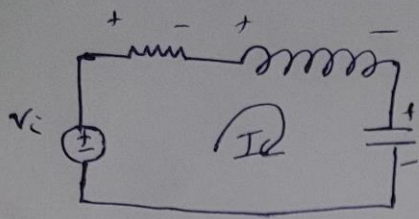

$$v_i = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt \quad (1)$$

$$\left[\begin{array}{l} \text{Applying Laplace transformation} \\ \frac{dx}{dt} = \frac{X(s)}{s} \end{array} \right]$$

$$v_i = RI(s) + sLI(s) + \frac{I}{sC} \quad (2)$$

$$v_o(s) = \frac{1}{sC} I(s) \quad (3)$$

$$(2) \div (3) \Rightarrow \frac{v_o}{v_i} = \frac{1/sC}{R + sL + 1/sC} \Rightarrow \frac{1}{s^2 LC + RCs + 1}$$

$$\approx \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + 1} \approx \frac{1/LC}{\frac{s^2 LC + RCs + 1}{LC}} \approx \frac{1/LC}{s^2 + R/L s + 1/LC}$$

$$\text{So, } \omega_n^2 = \frac{1}{LC} \Rightarrow \omega_n = \frac{1}{\sqrt{LC}}$$

$$2\zeta\omega_n = \frac{R}{L} \Rightarrow 2\zeta \frac{1}{\sqrt{LC}} = \frac{R}{L} \quad [\text{from } \omega_n = \frac{1}{\sqrt{LC}}]$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

[where ζ is damping ratio]

- if $\zeta > 1 \rightarrow$ overdamped
- $\zeta = 1 \rightarrow$ critically damped
- $\zeta < 1 \rightarrow$ underdamped
- $\zeta = 0 \rightarrow$ undamped

Case 1) $R = 50 \Omega$

$R_{eq} = 50 + 50 = 100 \Omega$

$$\xi_c = \frac{100}{2} \sqrt{\frac{6.2 \times 10^{-9}}{9.6 \times 10^{-7}}}$$

$\xi_c = 0.126$ so here $\xi_c < 1$

Percentage Peak overshoot

$$\therefore M(p) = \frac{C(t_p) - C_0}{C_0} = \frac{2.32 - 5}{5}$$

$$= 0.664$$

$$M(p) = 66.4\%$$

$$\therefore M(p) \text{ theoretical} = \frac{-\pi \xi_c}{e^{\sqrt{1-\xi_c^2}}} \times 100$$

$n=1$ for First peak

$$= \frac{-1 \times 3.14 \times 0.126}{e^{\sqrt{1-(0.126)^2}}} \times 100$$

$$= e^{-\frac{0.395}{6.90}} \times 100$$

$$= 0.67$$

$$\approx 67.1\%$$

Peak time is a time required for the response to reach the peak of

the response

$$t_p = \frac{\pi}{\omega \sqrt{1-\xi_c^2}} = \frac{1 \times 3.14}{4098.9 \sqrt{1-(0.126)^2}}$$

$$t_p = 7.91 \mu\text{sec}$$

$$T = 2t_p \Rightarrow T = 15.8 \mu\text{sec}$$

Time Constant

$$\tau = \frac{2L}{R_{eq}} = \frac{2 \times 9.63}{100} = 1.92 \times 10^{-4} \text{ sec}$$

Case 2: When $\xi = 1$, critical damped condition

$$\frac{R_{eq}}{2} \sqrt{\frac{C}{L}} = 1$$

$$R_{eq} = \frac{2 \times \sqrt{9.6 \text{ m}}}{\sqrt{1.2 \text{ n}}}$$

$$\boxed{R_{eq} = 787.4 \text{ } \Omega}$$

$$\text{so } R = 787.4 - 50 = 737.4 \text{ } \Omega$$

$$\% M(p) \text{ simulation} = \frac{S-S}{S} = 0$$
$$= 0\%$$

$$\% M(p) \text{ Theoretical} = \frac{-\pi \xi}{e^{\sqrt{1-\xi^2}}} \times 100$$
$$= \frac{1}{e^{\infty}} \times 100$$
$$= 0\%$$

$$\text{Peak time } t(p) = \frac{\pi}{\omega \sqrt{1-\xi^2}} = \infty$$

$$\text{Time Constant } \tau = \frac{2L}{R_{eq}} = \frac{2 \times 9.6 \times 10^{-3}}{787.4} = 2.43 \times 10^{-5} \text{ sec}$$

Case 3) $R = 200\Omega$, $R_{eq} = 200 + 50 = 250\Omega$

$$\xi = \frac{250}{2} \sqrt{\frac{6.27}{9.6}} = \frac{250 \times 12.53}{18 \times 100}$$

$$\xi = 0.31625 \text{ for } \xi \leq 1$$

$$\therefore \text{Peak } \gamma \cdot M(P)_{\text{simulator}} = \frac{674-5}{5}$$

$$\boxed{= 34.8\%}$$

$$\gamma \cdot M(P)_{\text{theoretical}} = \frac{-1 \times \xi}{e^{\sqrt{1-\xi^2}} \times 100}$$

$$= \frac{-1 \times 3.14 \times 0.316}{e^{\sqrt{1-(0.316)^2}} \times 100}$$

$$= \frac{-0.992}{e^{0.948} \times 100}$$

$$\approx 35.2\%$$


Peak time;

$$t_p = \frac{\pi}{\omega \sqrt{1-\xi^2}} = \frac{1 \times 3.14}{40989 \sqrt{1-(0.316)^2}} = \frac{3.14}{38957.57}$$


$$\boxed{t_p \approx 8.087 \times 10^{-5} \text{ ms}}$$

$$\text{Time constant } (T) = 7.68 \times 10^{-5} \text{ sec}$$


Circuit Diagram and Link:

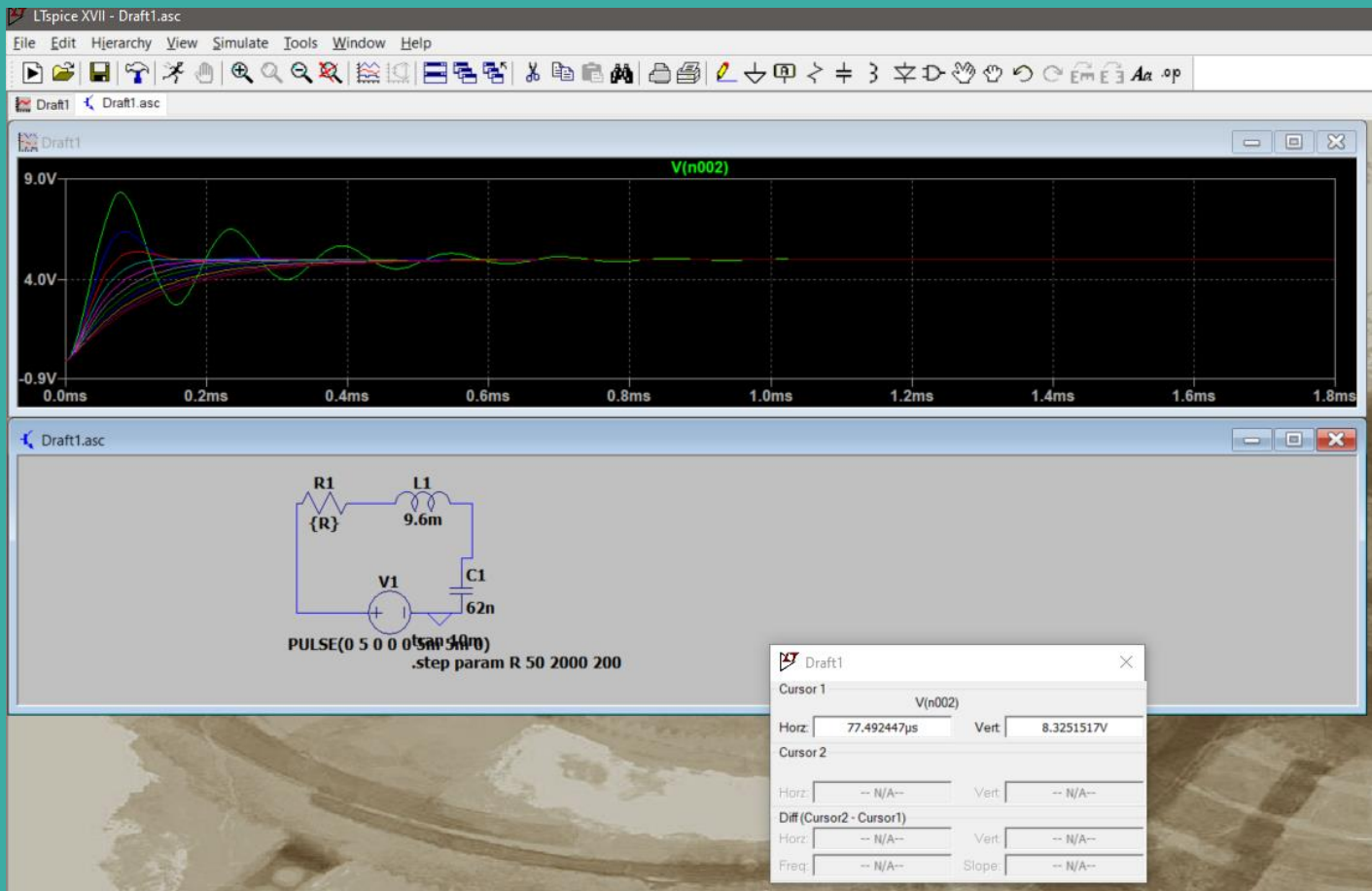


R=50ohm

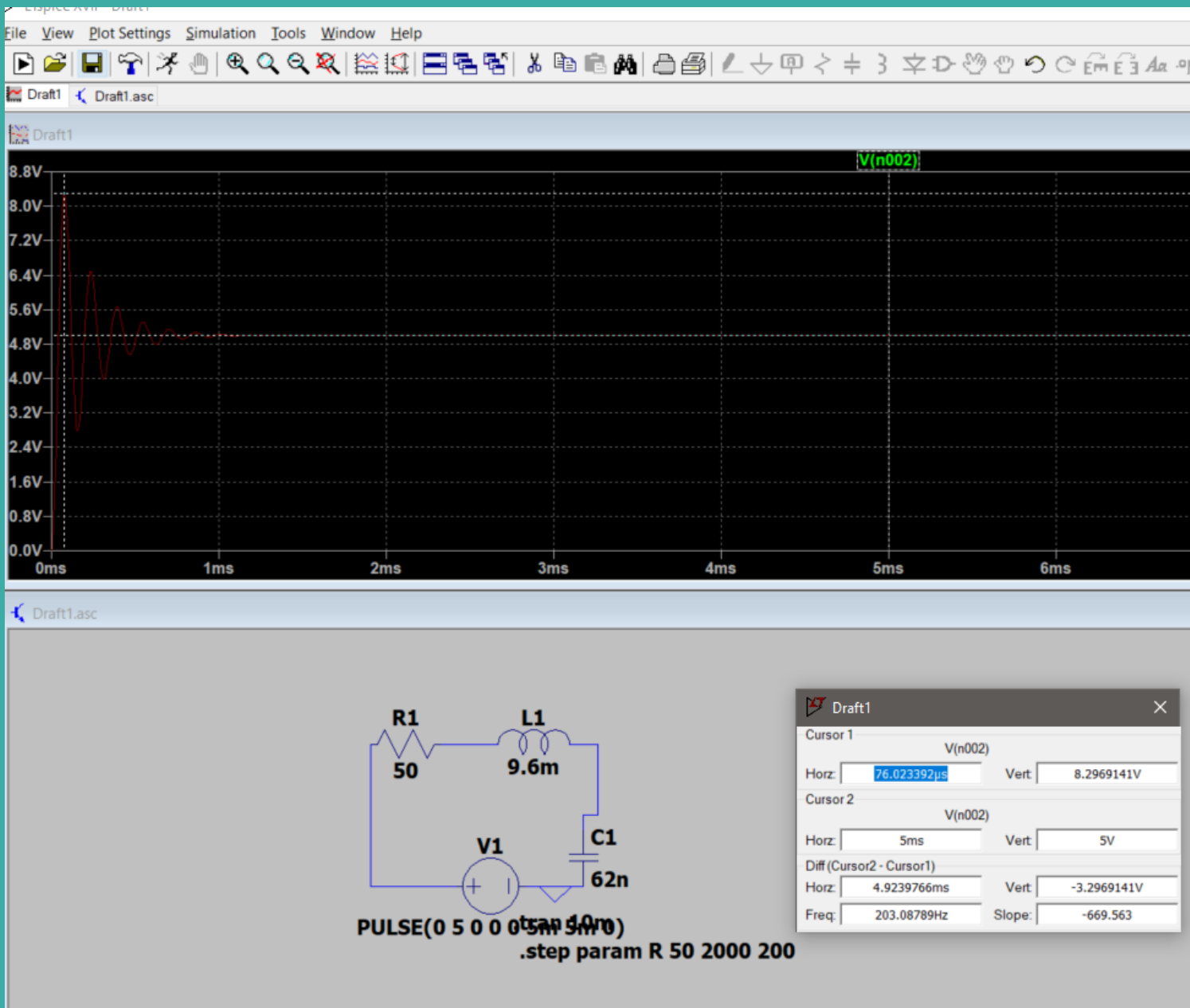

R= 787.4ohm

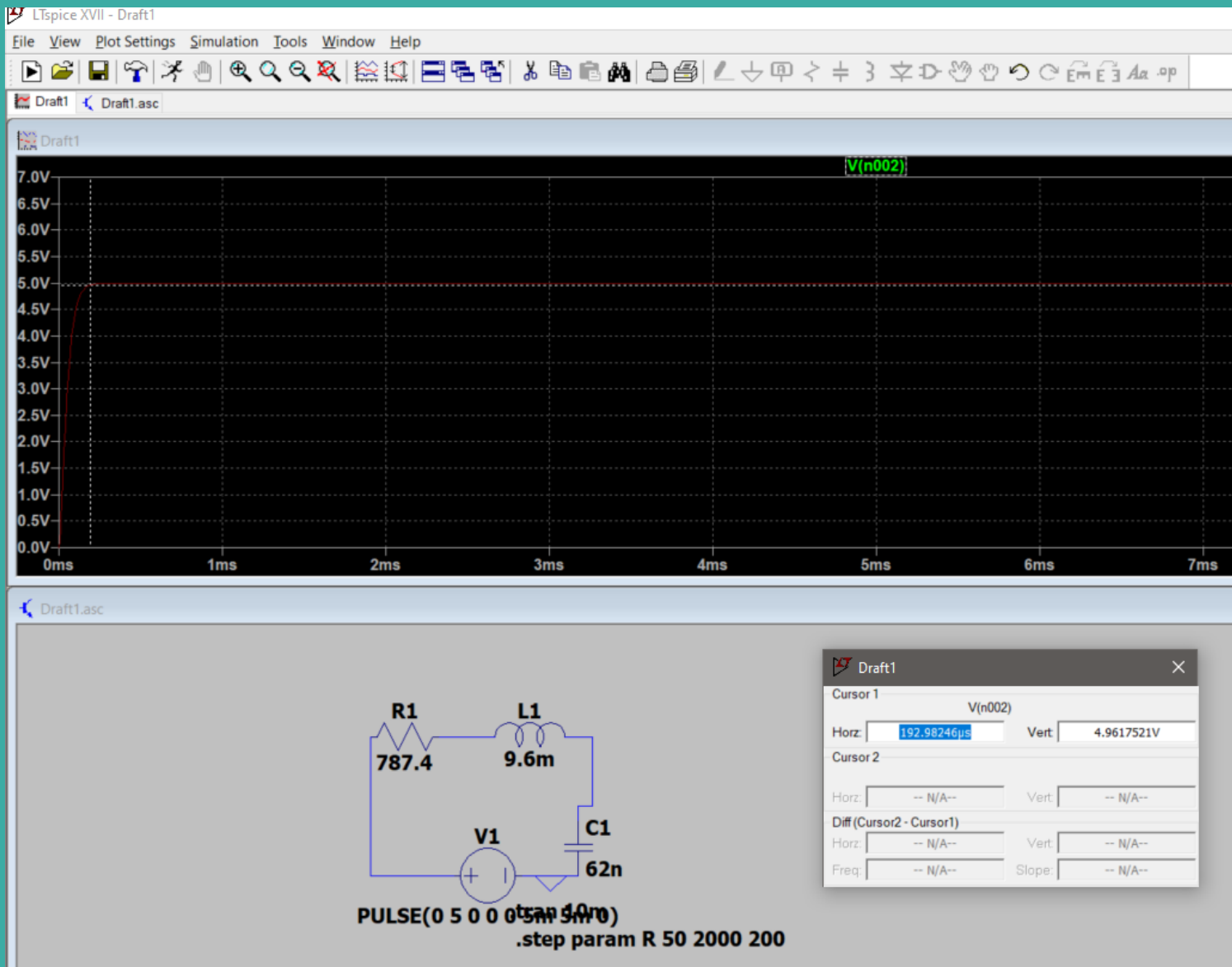

R= 200ohm

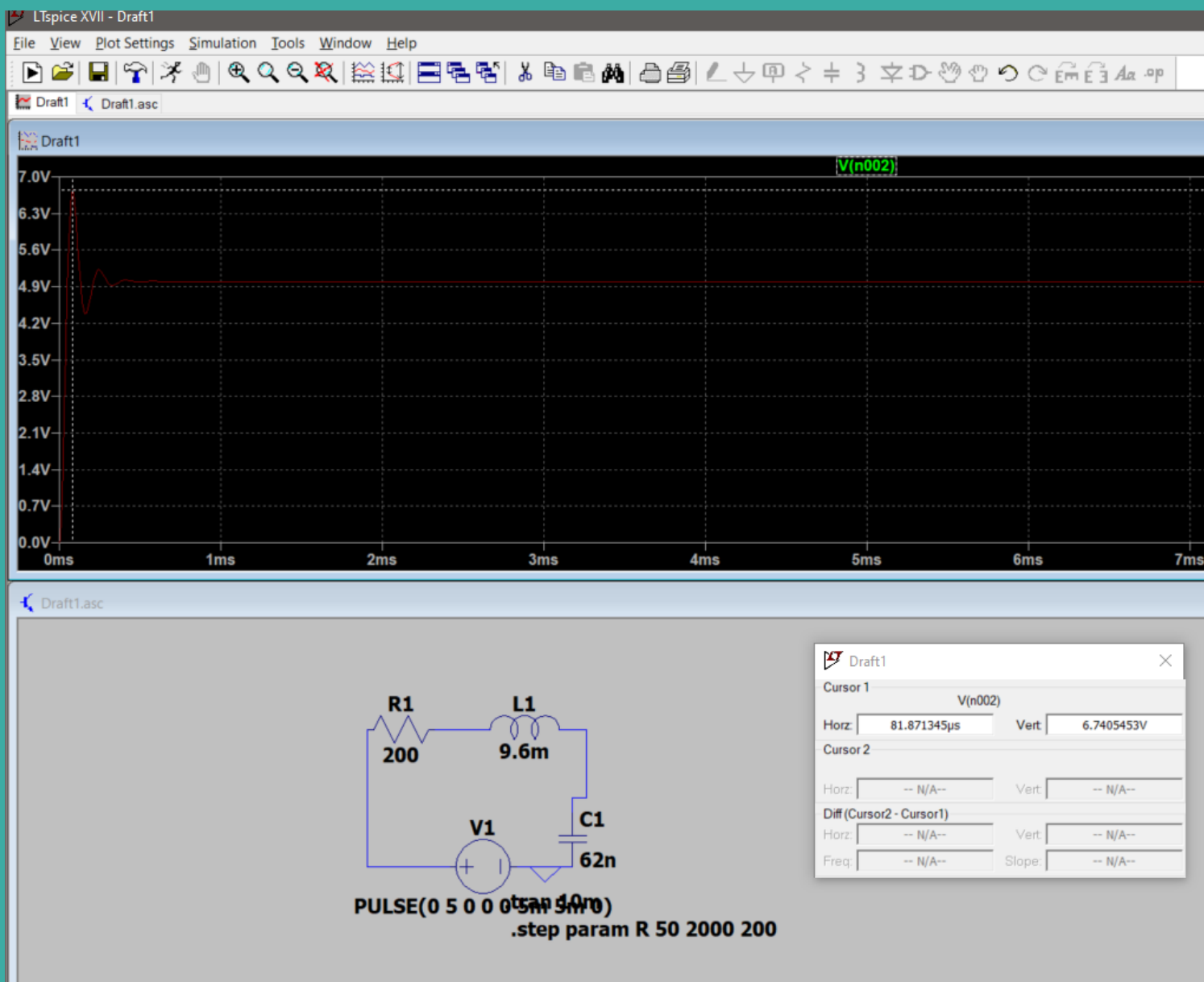

Observations/Results:

After doing observing period of oscillation, time constant and peak overshoot and comparing this value with theoretically calculated values we found they are nearly same

Applications:

- It is used to detect the frequencies of the narrow range in the broad spectrum of radio waves.
- It is used to tune radio frequency of AM/FM radio