



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

Department  
of  
Electronics & Communication Engineering

ECE113|Basic Electronics

Lab :2

Student Name: Dheeraj  
Roll No.:2020194  
Date:27-06-21

**Aim:** 1) Verify Thevenin's and Norton's equivalent representations using Virtual Labs.  
2) To verify maximum power transfer theorem and superposition theorem using Virtual labs.


**Components:** Power supply, Amperage Multimeter, resistor, wires.

Software/Tools Used :

- TinkerCad
- Virtual Labs

**Theoretical Calculation :**

# Lab-3

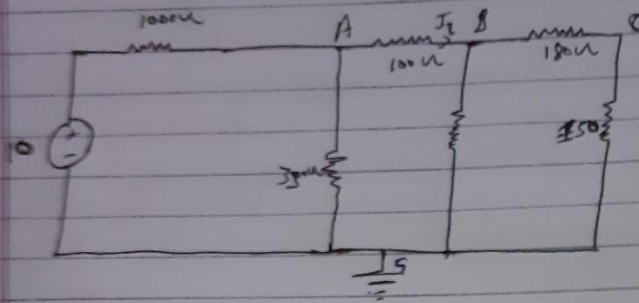


$$\begin{array}{r} 150 \\ 180 \\ \hline 330 \end{array}$$

$$\begin{array}{r} 1000 \\ 330 \\ \hline 1330 \end{array}$$

$$V_0 = \frac{10 \times 1000}{1330}$$

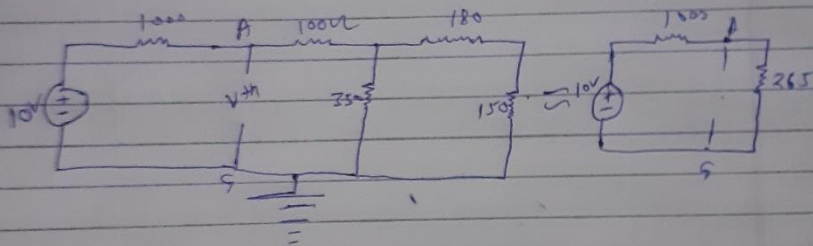Finding  $V_{th}$  so opening the load resistance  $R_L$  i.e.  $45\Omega$  Node




$$V_{th} = I \times \frac{10}{1.265} = 7.904 \text{ mV}$$

$$V_{th} = I \times 265$$

$$= 7.904 \times 10^{-3} \times 265$$


$$V_{th} = 2.094 \text{ V}$$

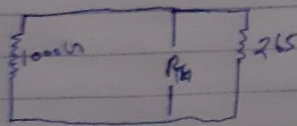

$$R_{th} = \frac{265 \times 1000}{265 + 1000}$$

$$R_{th} = 209.486 \Omega$$

### Thevenin's circuit

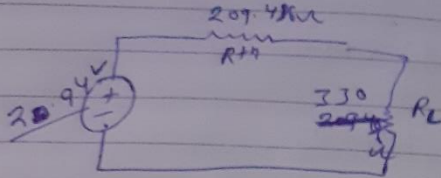

$$P = i^2 \times R \quad [i = 3.88 \text{ mA}]$$

$$P = \left(\frac{3.88}{1000}\right)^2 \times 330$$

$$P = 4.96 \text{ mW}$$

Ques 1)  $R_L = 209.486 = R_{TH}$

$$P = i^2 \times R = \left(\frac{5}{100}\right)^2 \times 209.481$$

$$P = 5.25 \text{ mW}$$

$$P_{max} = \frac{V_{th}^2}{4R_{TH}} = \frac{(2.094)^2}{4(209.486)} \approx 5.24 \text{ mW}$$

Thus verified Max power is when  $R_{TH} = R_L$  are equal

Ques 2)  $R_L = 50 \Omega$

$$P = i^2 \times R = \left(\frac{18.07}{1000}\right)^2 \times 50 = 3.26 \text{ mW}$$

Date: / /

Case 4:  $R_L = 400 \Omega$

$$P = i^2 R = \left( \frac{3.44}{1000} \right)^2 \times 400$$


$$P = \cancel{1.25} \quad 4.71 \text{ mW}$$

Case 5:  $R_L = 250 \Omega$

$$P = i^2 R = \left( \frac{8.93}{1000} \right)^2 \times 25$$


$$P = \cancel{2.23 \text{ mW}} \quad 1.99 \text{ mW}$$

Hence Verified

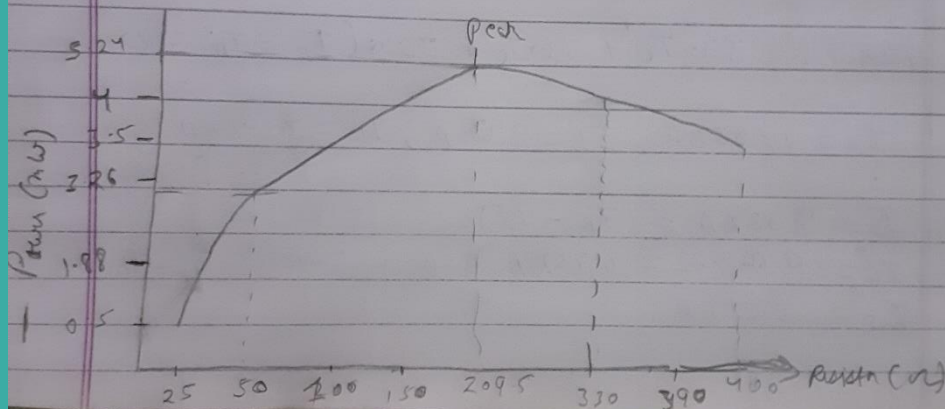

**Superposition theorem:**

2) Verification of superposition theorem

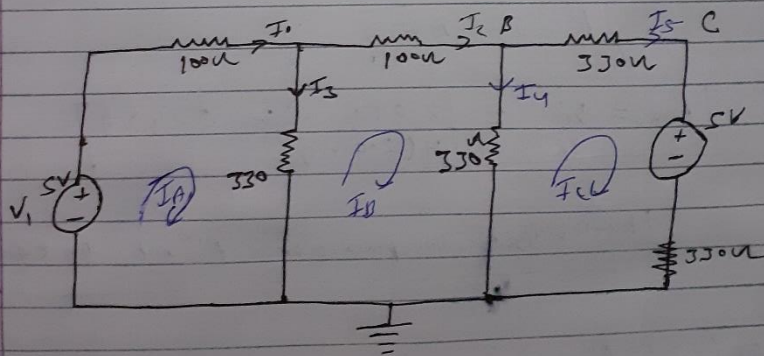

Case 1)  $V_1 = 5$ ,  $V_2 = 5V$

Mesh 1:  $5 = 100I_1 + 330(I_1 - I_2)$  — (1)

Mesh 2:  $100I_2 + 330(I_2 - I_1) + 330(I_2 - I_3) = 0$  (2)

Mesh 3:  $330I_3 + 330I_3 + 330(I_3 - I_2) = -5$  (3)



from ① ② ③ after solving;

$$I_A = 15.826 \text{ mA}$$

$$I_C = -3.22 \text{ mA}$$

$$I_B = 5.47 \text{ mA}$$

$$I_3 = 15.826 - 5.47 = 10.356 \text{ mA} \quad [I_A - I_B]$$


$$I_3 = 10.356 \text{ mA}$$

$$I_4 = I_B + I_C = 5.47 + 3.22$$

$$I_4 = 8.67 \text{ mA}$$

$$I_5 = -3.22 \text{ mA}$$

(Q4 2)  $V_1 = 5 \text{ V}$ ,  $V_2 = 0$

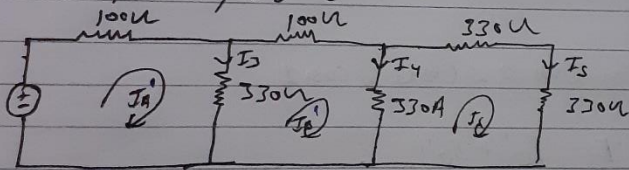

Mesh 1:  $5 = 100I_A + 330(I_A - I_B)$

Mesh 2:  $100I_B + 330(I_B - I_C) + 330(I_B - I_A) = 0$

Mesh 3:  $330I_C + 330I_C + 330(I_B - I_A) = 0$


$$I_A = 19.65 \text{ mA}, I_B = 9.6 \text{ mA}, I_C = 3.22 \text{ mA}$$

$$I_3 = 9.38 \text{ mA} \quad [I_A - I_B]$$

$$I_4 = 9.6 - 3.22 = 6.45 \text{ mA}$$

$$I_5 = 3.22 \text{ mA}$$

Case 3:  $V_1 = 0$ ,  $V_2 = 5V$

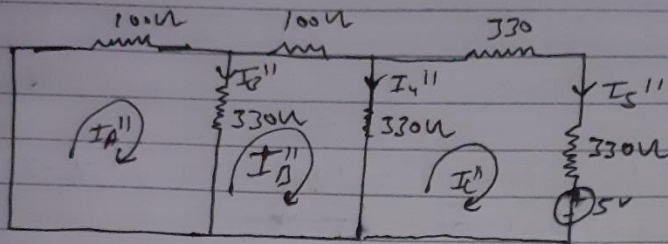

Mesh 1:  $0 = 100I_A'' + 330(I_A'' - I_D'')$

Mesh 2:  $100I_A'' + 330(I_D'' - I_C'') + 330(I_D'' - I_S'') = 0$

Mesh 3:  $330I_C'' + 330I_C'' + 330(I_C'' - I_A'') = -5$

$I_A'' = -3.22mA$ ,  $I_D'' = -4.20mA$

$I_C'' = 6.45mA$

so  $I_3'' = 0.98mA$ ,  $I_4'' = +2.25mA$ ,  $I_5'' = -6.45mA$

From Case 2 & Case 3 & Case 1

$I_3 = I_3' + I_3''$

$I_4 = I_4' + I_4''$

$I_5 = I_5' + I_5''$



Hence Verified



Circuit Diagram and Link:


Maximum power transfer Theorem



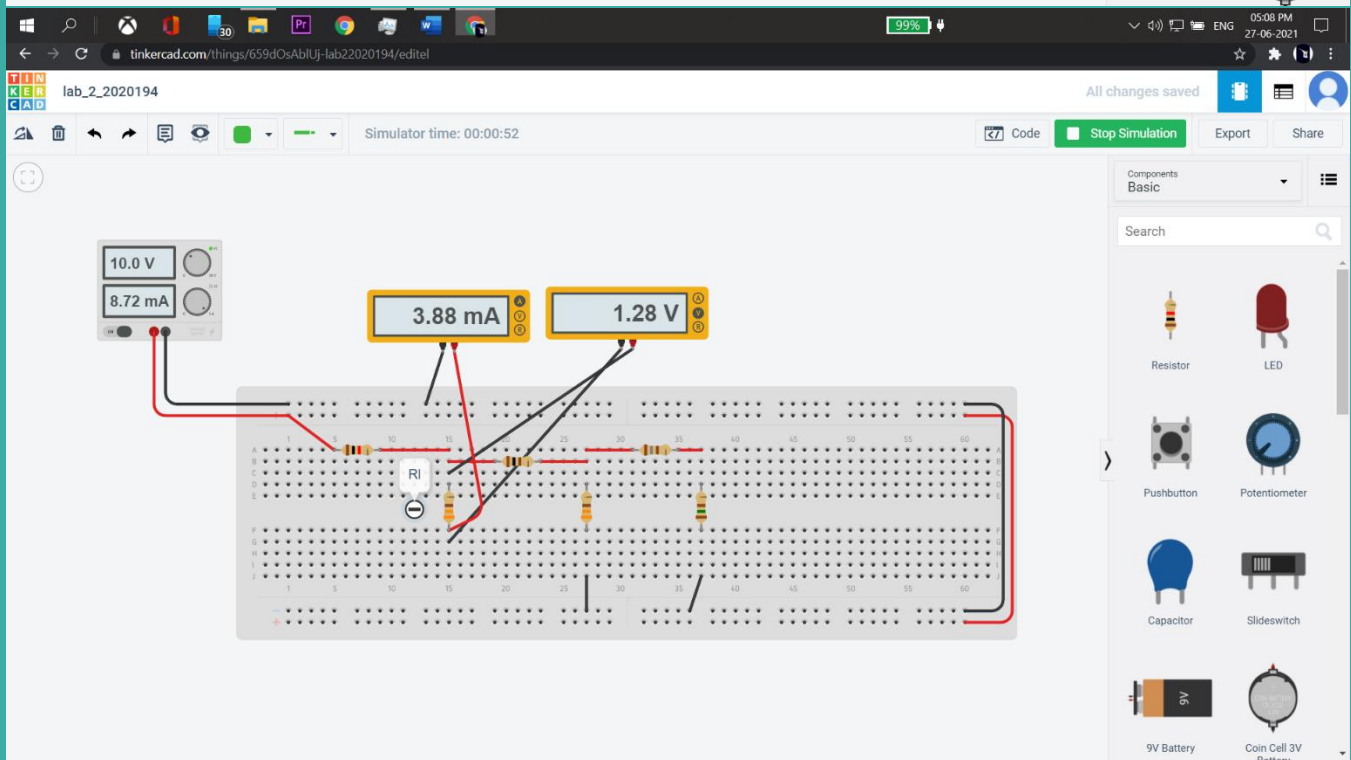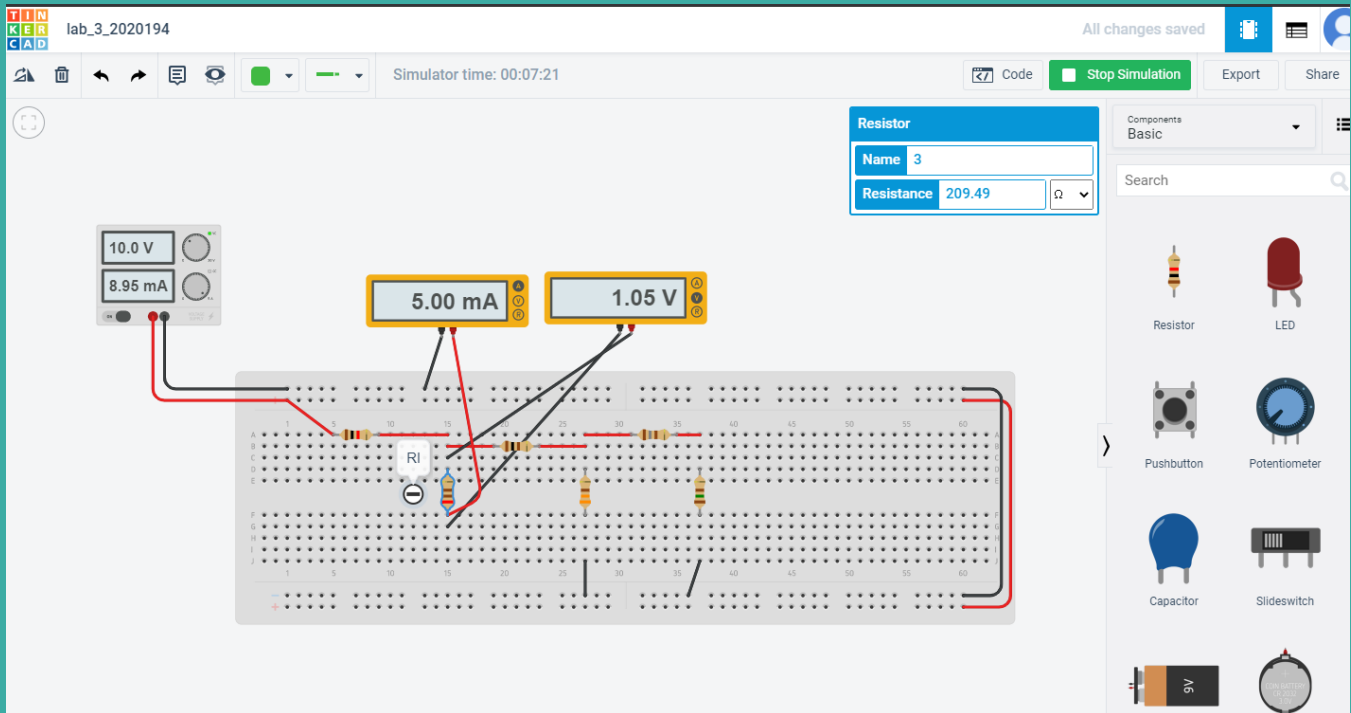[https://www.tinkercad.com/things/659dOsAbIUj-lab22020194/editel?sharecode=lsW58uNqDIzOCjc\\_Lb9LfqXZMBDM\\_ustYrafxZMirm8](https://www.tinkercad.com/things/659dOsAbIUj-lab22020194/editel?sharecode=lsW58uNqDIzOCjc_Lb9LfqXZMBDM_ustYrafxZMirm8)




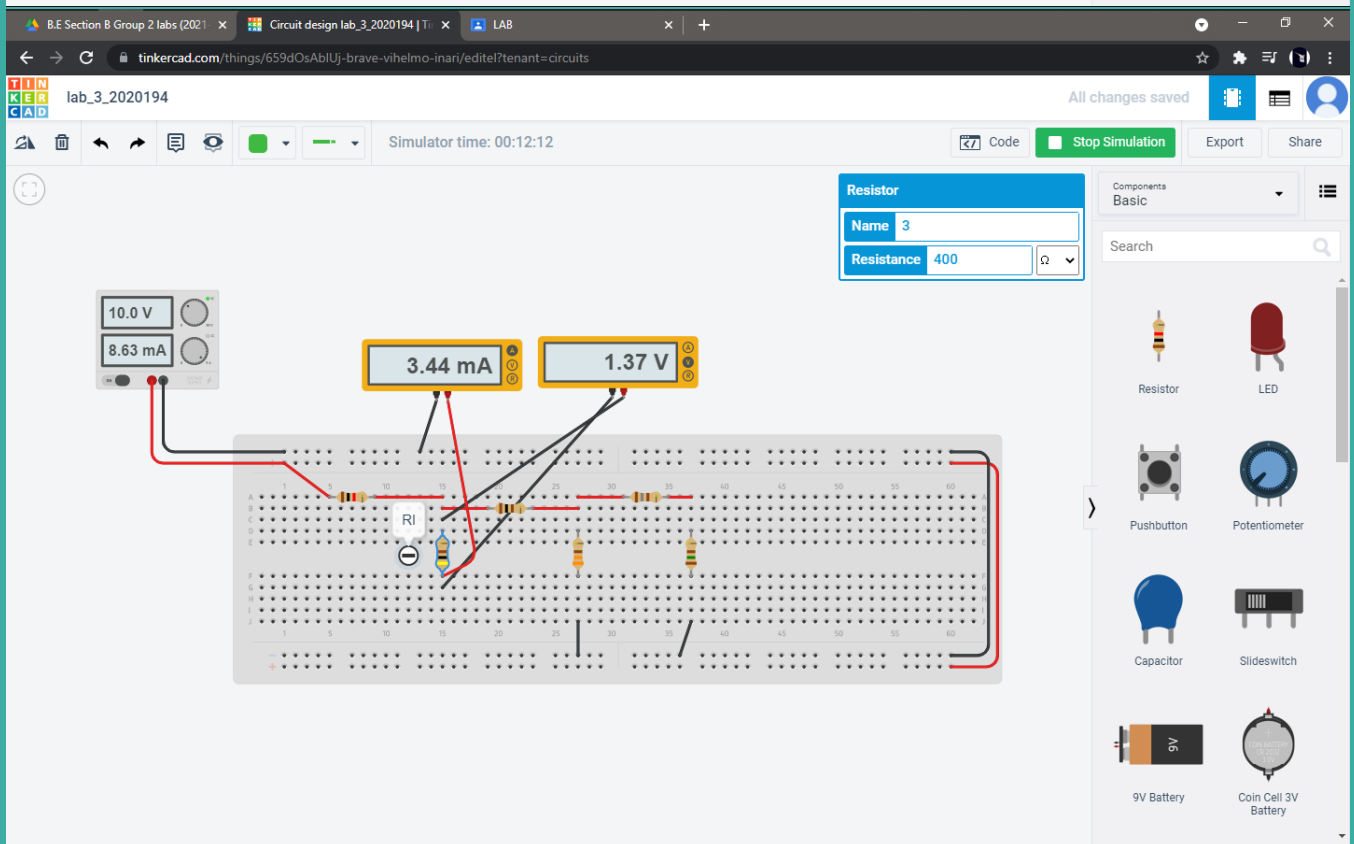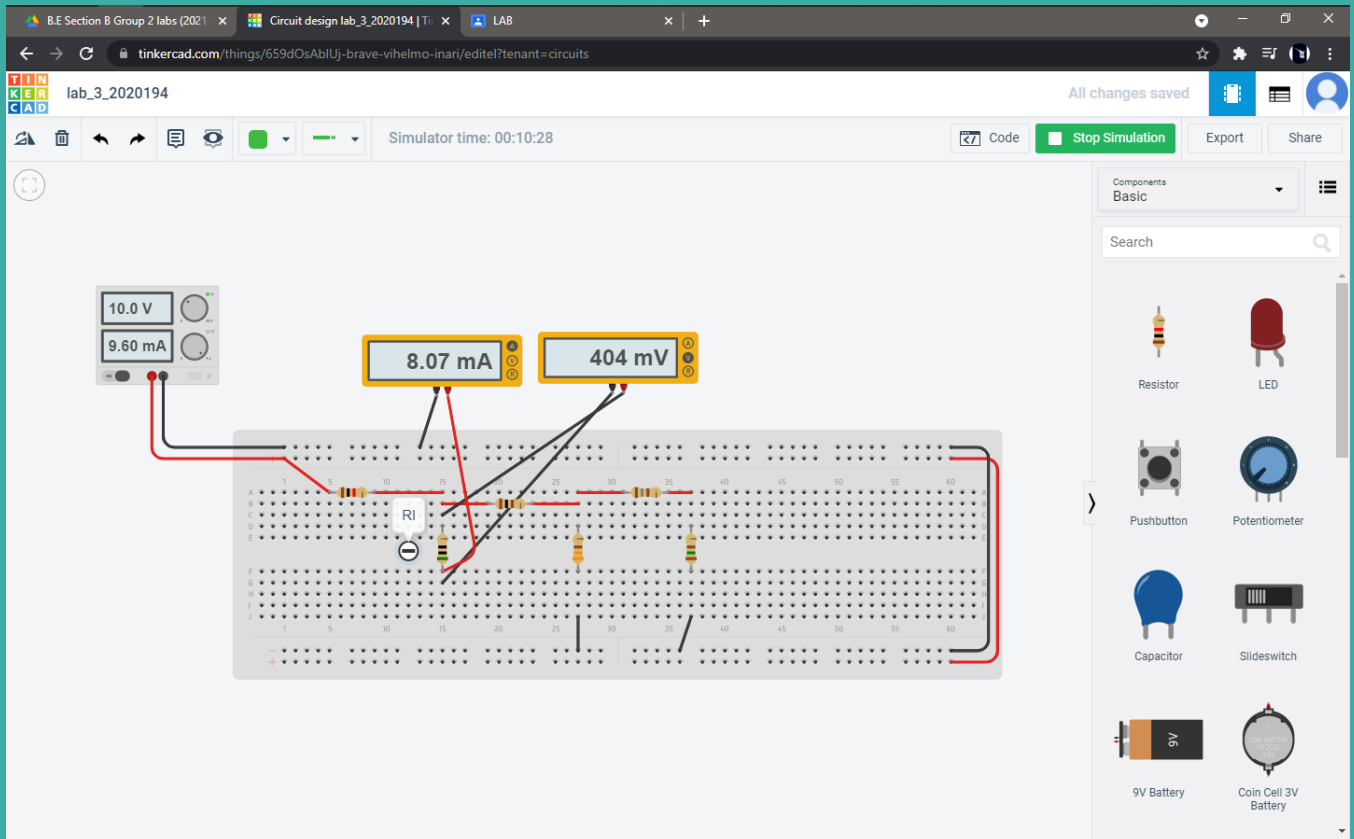

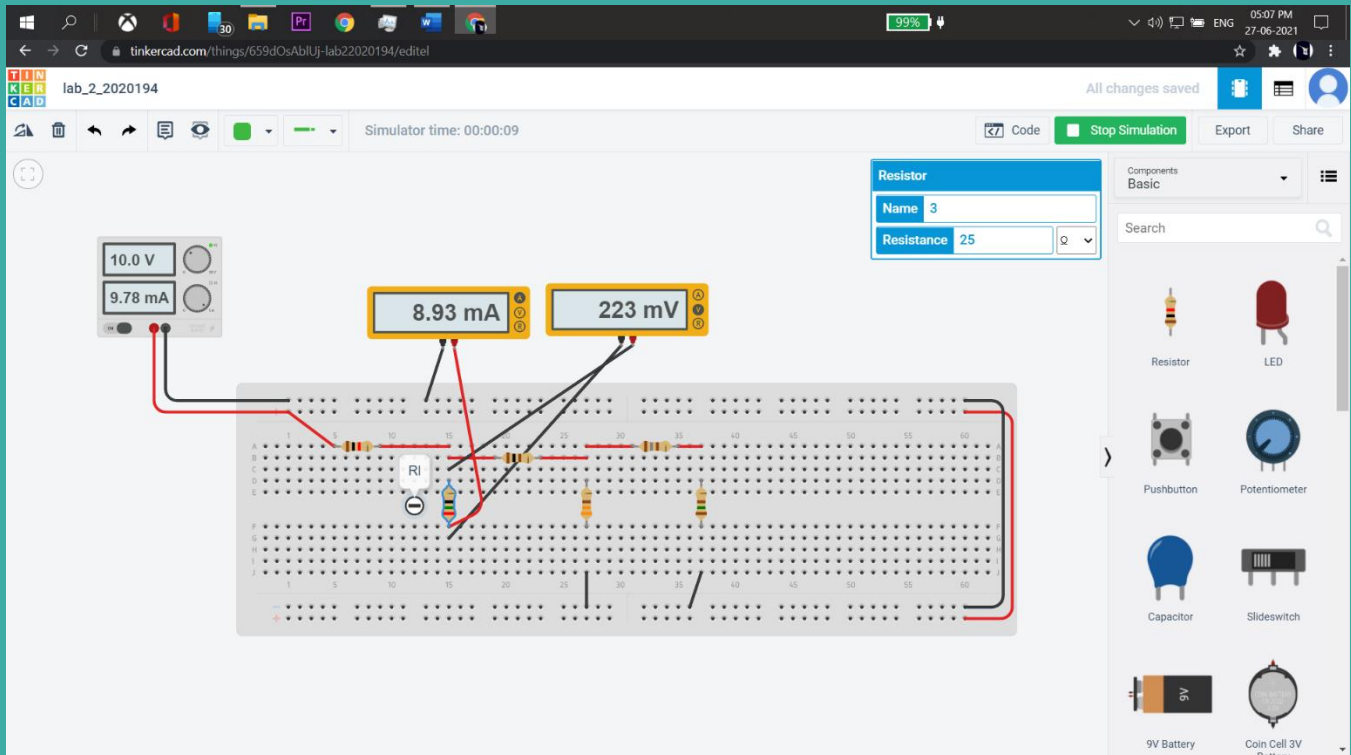

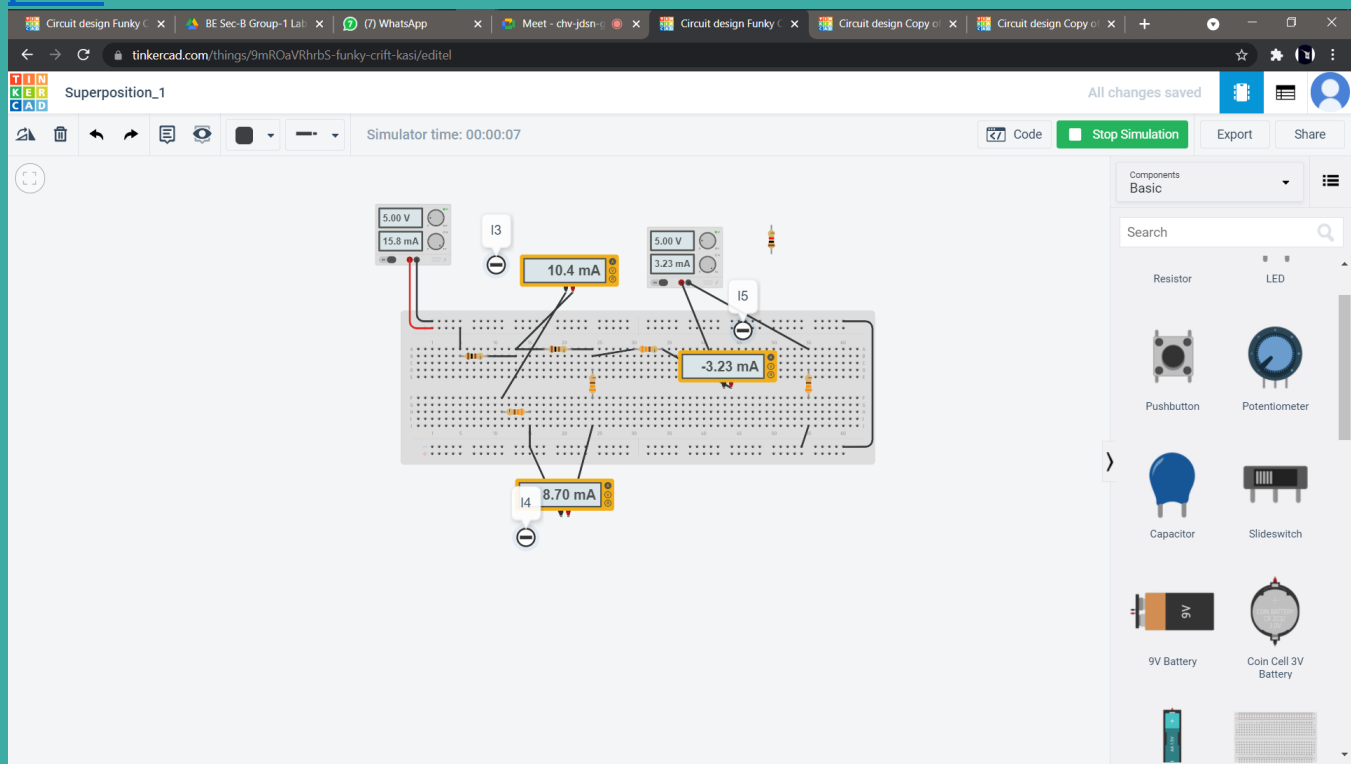
## Superposition Theorem


[https://www.tinkercad.com/things/9mROaVRhrbS-funky-crif-kasi/editel?sharecode=uDqcy2KZE7yMD\\_lmOHIA9O1qoiHNMNF3TJQI2-](https://www.tinkercad.com/things/9mROaVRhrbS-funky-crif-kasi/editel?sharecode=uDqcy2KZE7yMD_lmOHIA9O1qoiHNMNF3TJQI2-)


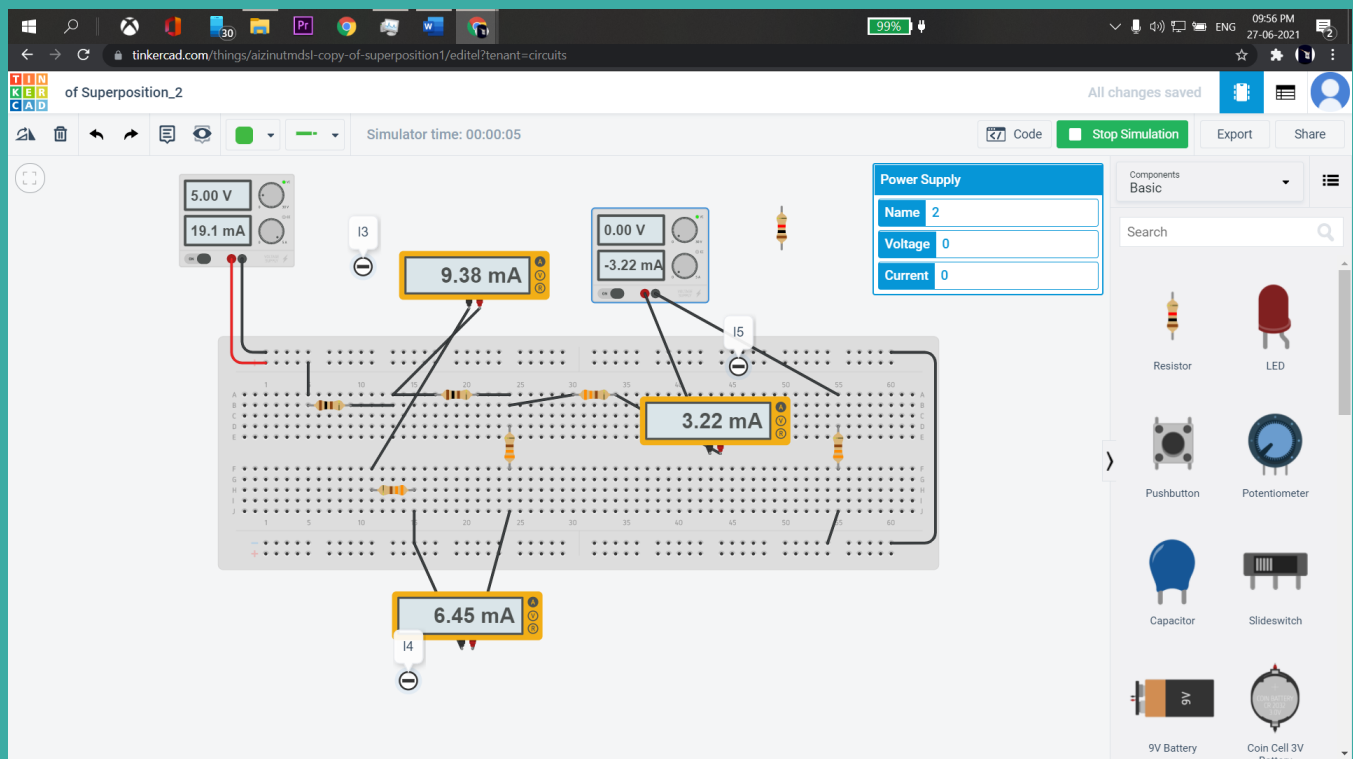
<https://www.tinkercad.com/things/aizinutmdsl-copy-of-superposition1/editel?sharecode=1-QF-sndk2MYu7fb5kJ1-n2TgqJzr8OGOqr1DJ6c7xs>




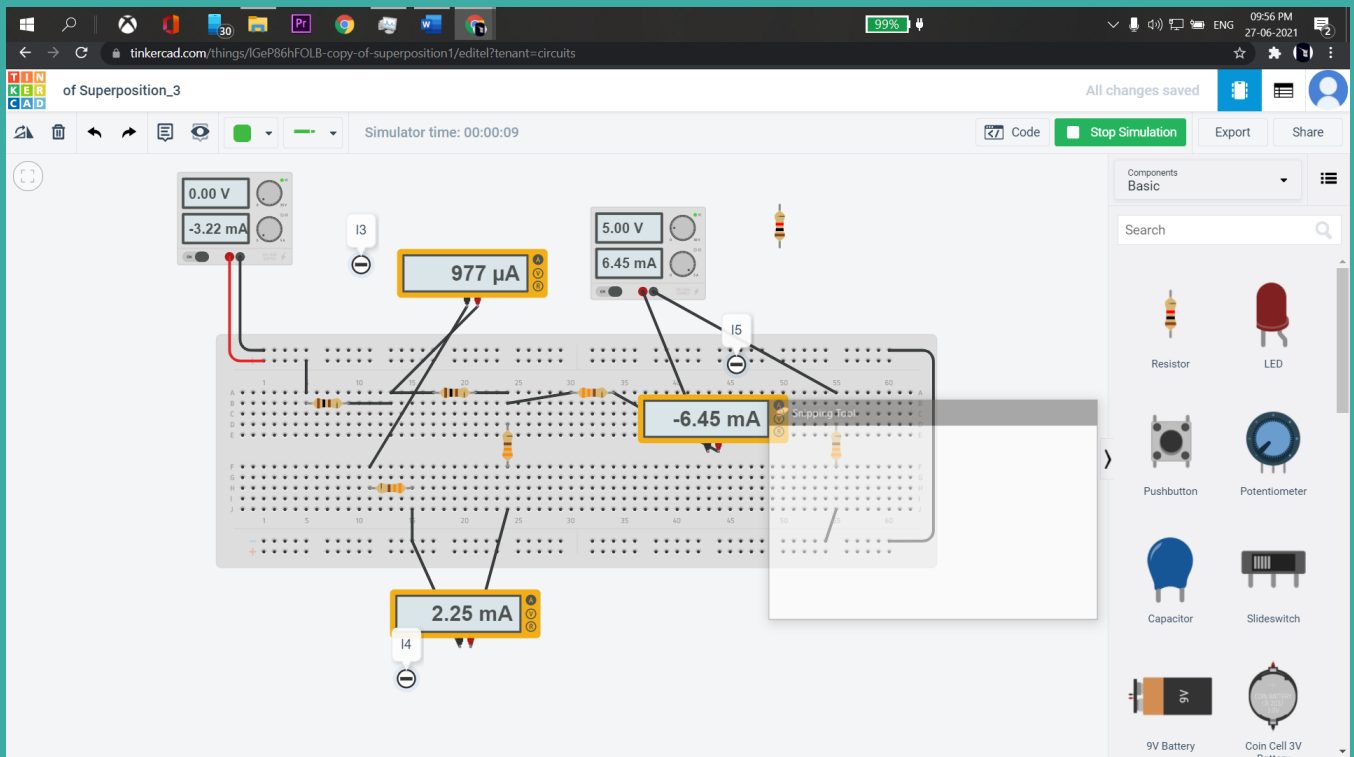[https://www.tinkercad.com/things/lGeP86hFOLB-of-superposition3/editel?sharecode=rVnS0mBBxDKWmyZyT7jFaKe5CUCAC\\_ANpJ48YYBsNLY](https://www.tinkercad.com/things/lGeP86hFOLB-of-superposition3/editel?sharecode=rVnS0mBBxDKWmyZyT7jFaKe5CUCAC_ANpJ48YYBsNLY)



V<sub>LAB</sub>:



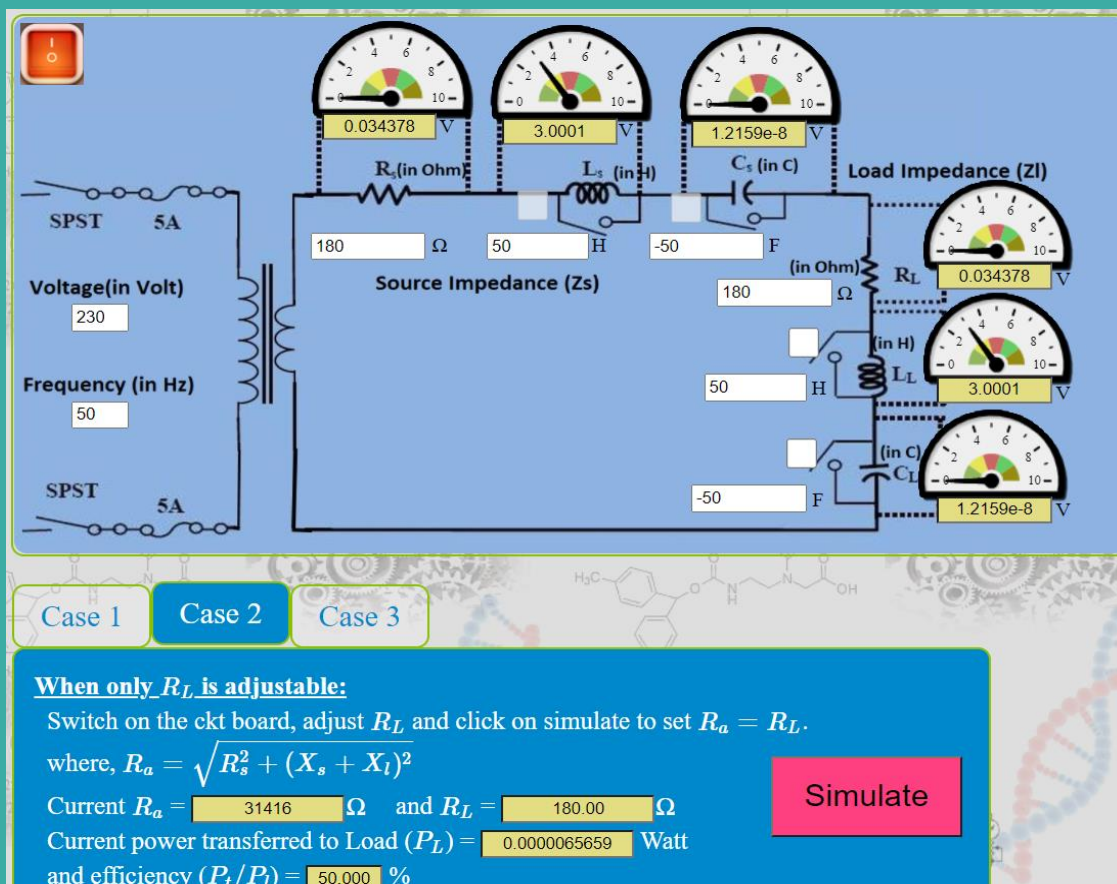

## OBSERVATION Table:

### Maximum power transfer Theorem:

Sno	RI	IL	Power= $I_L^2 \cdot R_L$	Vth
1	209.486ohm	5mA	5.25mW	1.05v
2	330ohm	3.88mA	4.96mW	1.28v
3	50ohm	8.07mA	3.26mW	404mV
4	400ohm	3.44mA	4.71mW	1.37v
5	25ohm	8.93mA	1.99mW	223mv

## Superposition Theorem :

Sno.	V1	V2	I3	I4	I5
1	5v	5v	10.356mA	8.67mA	-3.22mA
2	5v	0	9.38mA	6.45mA	3.22mA
3	0	5v	-3.22		

## V LAB OBSERVATION TABLE:

### Superposition Theorem

Serial no. of Observation	In presence of both $V_1$ and $V_2$			In presence of $V_1$ only			In presence of $V_2$ only		
	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)
1st	0.39032	-0.10645	0.28387	0.56774	-0.35484	0.21290	-0.17742	0.24839	0.070968
2nd	0.25385	-0.016923	0.23692	0.33846	-0.16923	0.16923	-0.084615	0.15231	0.067692
3rd	0.15316	0.041772	0.19494	0.22278	-0.13924	0.083544	-0.069620	0.18101	0.11139
4th	0.62857	-0.23571	0.39286	0.94286	-0.62857	0.31429	-0.31429	0.39286	0.078571
5th	0.16923	0.084615	0.25385	0.28205	-0.22564	0.056410	-0.11282	0.31026	0.19744

**Observations/Results:** Maximum power transfer occurs when the Thevenin Resistance ( $R_{th}$ ) is equal Load resistance ( $R_L$ ) of the circuit.

The current in each branch of a circuit is equal to the contribution of each voltage source and/or current source taken independently.

We verified max power transfer theorem and superposition theorem

### Applications:

- communications systems, maximum power power is always preferred.

- Superposition theorem can be applied when we have to calculate the current across a specific branch containing several current/voltage sources