

- $E(t)$ is the external voltage provided to circuit. Here, $E(t) = E_0 \sin(\omega t)$.
- Relationship in the capacitor between charge and current is

$$I = \frac{dQ}{dt}$$

Q.1 Write a 2nd order ODE model for the current $I(t)$ in this RLC circuit.

Q.2 Solve the characteristic eq. of homogeneous part (find roots in terms of R, L & C).

or From Kirchhoff's law

$$\Rightarrow E_0 \sin(\omega t) - IR - \int I \cdot dt - L \cdot \frac{dI}{dt}$$

$$\Rightarrow E_0 \cdot \omega \cdot C \cos(\omega t) - I'R - \frac{I}{C} - L \cdot I'' = 0$$

or Now

$$L \cdot I'' + I'R + \frac{I}{C} = 0$$

$$L \cdot \lambda^2 + R \cdot \lambda + \frac{1}{C} = 0 \Rightarrow \lambda = \frac{-R \pm \sqrt{R^2 - 4LC}}{2L}$$

Q.1*) $y_p = a \cos \omega t + b \sin \omega t$

$$y_p' = -a\omega \sin \omega t + b\omega \cos \omega t$$

$$y_p'' = -a\omega^2 \cos \omega t - b\omega^2 \sin \omega t$$

$$\text{ODE} \Rightarrow L I'' + R I' + \frac{I}{C} = \omega E_0 \cos \omega t$$

Comp

$$\omega E_0 = R\omega b + a - a\omega^2 L$$

$$0 = b - aR\omega - \omega^2 Lb$$

$$E_0 = Rb + a(-\omega L + \frac{1}{C\omega}) \quad \text{--- (1)}$$

$$0 = b\left(\frac{1}{C\omega} - L\omega\right) - Ra \quad \text{--- (2)}$$

$$\text{let } s = -L\omega + \frac{1}{C\omega}$$

equations: $s_a + Rb = E_0$
 $s_b - Ra = 0$

$$s_b = Ra$$

$$b = \frac{R}{s} a \rightarrow \text{put in eq}$$

$$sa + \frac{R^2}{s} a = E_0 \Rightarrow a\left(s + \frac{R^2}{s}\right) = E_0$$

$$a\left(\frac{s^2 + R^2}{s}\right) = E_0$$

$$a = \frac{-sE_0}{R^2 + s^2}$$

$$b = E_0 R / (R^2 + s^2)$$

Q.2*) $y_p = a \cos(\omega t) + b \sin(\omega t)$

A.T.T. $y_p = C \cos(\omega t)$